 


Lab 02

GCD Engine

Due on Oct 16th 2016 11:59pm

黃稚存




Department of Computer Science
National Tsing Hua University

Description





- Calculate the greatest common divisor (GCD) of two 8-bit positive integers
- Using a START signal to load inputs
- Generate a DONE signal to indicate the result
- Assert an ERROR signal when one or more inputs are zero
- Note: this is not a full-featured design
 - Only a simple example
 - Do not copy & paste it into your research work

IO Specification


 


- Inputs:
 - *CLK*: clock source
 - *RST_N*: reset (low active)
 - *START*: to trigger the calculation
 - A one-cycle pulse to indicate the valid input numbers
 - *A, B*: two 8-bit input numbers
- Outputs:
 - *Y*: the result
 - *DONE*: to indicate the valid output with one-cycle pulse
 - *ERROR*: to indicate an error
 - 0: normal result
 - 1: invalid when $A = 0$ or $B = 0$


Primary IOs and Block Diagram

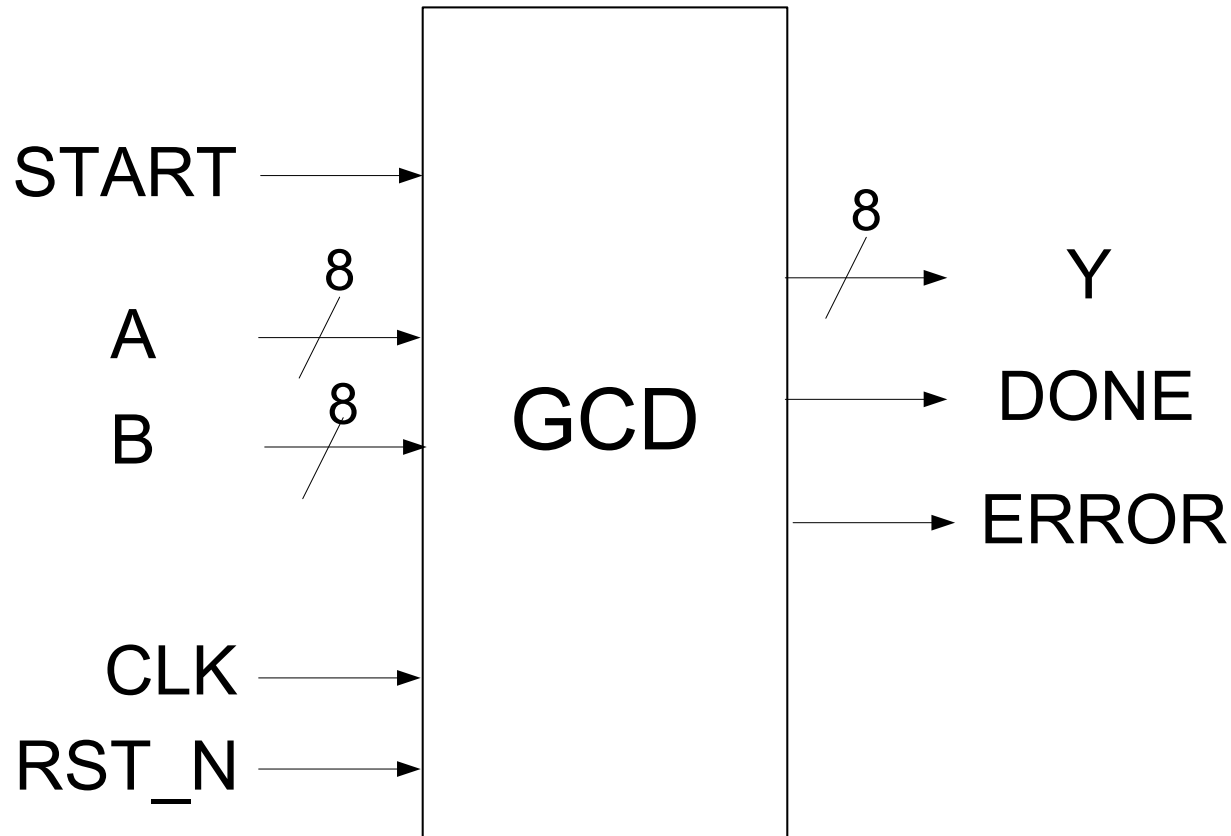 



Finite State Machine (Control)

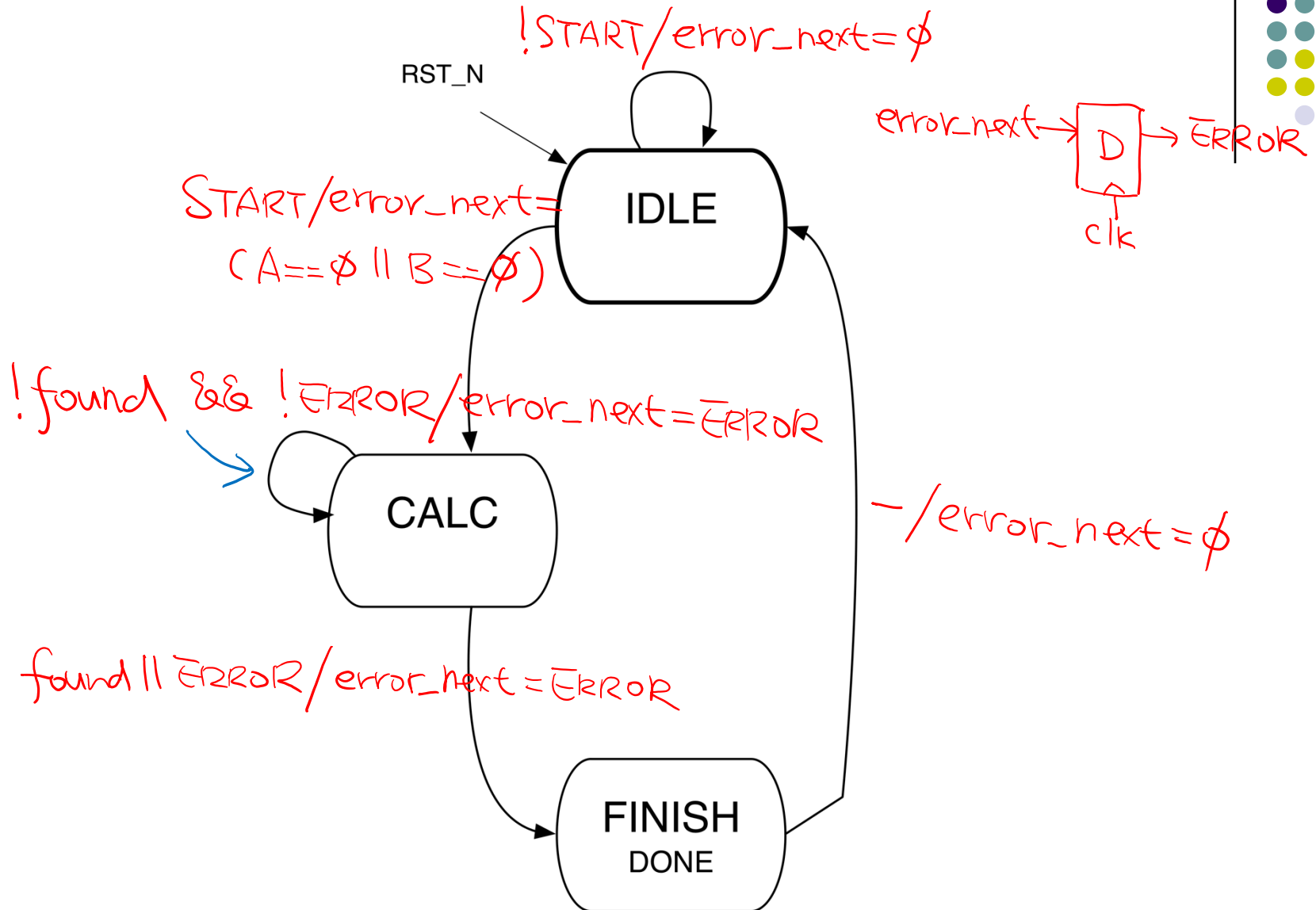 



Timing Diagram – Normal Operation

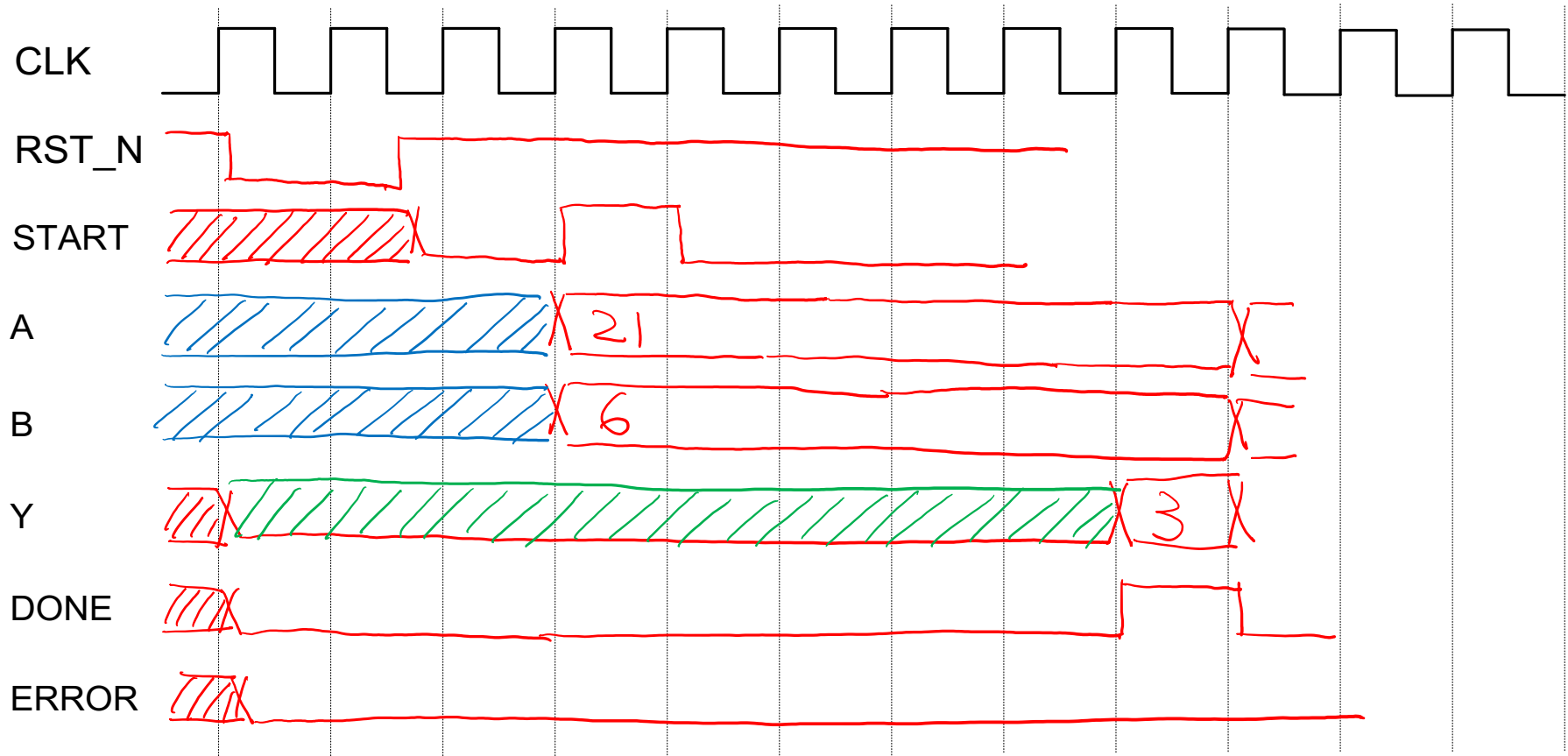

Timing Diagram – Error

  

Overall Architecture (Block Diagram)

  


$\text{Swap} = (\text{reg_b} > \text{reg_a}) ? 1'b1 : \phi;$

$\text{found} = (\text{reg_a} == \text{reg_b} \parallel A == B) ?$


$1'b1 : \phi;$

Design Procedure

 

- Start with spec, primary I/Os, and block diagram
- Design the overall architecture
- Specify finite state machine(s), data path, and internal signals
- List the timing diagrams of major operations
- Verilog coding
- Prepare comprehensive test environment for efficient debugging

Lab Template: Makefile

 

```
VLOG      = ncverilog
SRC        = gcd_t.v \
             gcd.v
VLOGARG    = +access+r

TMPFILE    = *.log \
             ncverilog.key \
             nWaveLog \
             INCA_libs

DBFILE     = *.fsdb *.vcd *.bak

RM         = -rm -rf
```


```
all :: sim

sim :
    $(VLOG) $(SRC) $(VLOGARG)

clean :
    $(RM) $(TMPFILE)

veryclean :
    $(RM) $(TMPFILE) $(DBFILE)
```


Lab Template: gcd.v (1/3)

 


```
module GCD (  
    input wire CLK,  
    input wire RST_N,  
    input wire [7:0] A,  
    input wire [7:0] B,  
    input wire START,  
    output reg [7:0] Y,  
    output reg DONE,  
    output reg ERROR  
);  
  
wire found, err, swap;  
reg [7:0] reg_a, reg_b, data_a, data_b;  
reg [7:0] diff;  
reg error_next;  
reg [1:0] state, state_next;  
  
parameter [1:0] IDLE = 2'b00;  
parameter [1:0] CALC = 2'b01;  
parameter [1:0] FINISH = 2'b10;
```

```
// [lab] define the signal found here  
//     assign found =  
// [lab] define the signal swap here  
//     assign swap =  
  
always @* begin  
    if (swap) begin  
        data_a = reg_b;  
// [lab] define the signal data_b here  
//     data_b =  
    end else begin  
// [lab] finish this block  
//     data_a =  
//     data_b =  
    end  
end  
  
always @* begin  
// [lab] finish this block  
//     diff =  
end
```

Lab Template: gcd.v (2/3)

 
 
```
always @(posedge CLK or negedge RST_N)
begin
// [lab] finish this sequential block
//     to describe Y
//
end
```



```
always @(posedge CLK or negedge RST_N)
begin
    if (~RST_N) begin
        reg_a = 0;
        reg_b = 0;
    end else if (START) begin
// [lab] finish this sequential block
//     to describe reg_a and reg_b
//
    end
end
```


Lab Template: gcd.v (3/3)



```
always @(posedge CLK or negedge RST_N) begin
    if (RST_N == 0) begin
        state <= IDLE;
        ERROR <= 0;
    end else begin
        state <= state_next;
        ERROR <= error_next;
    end
end
// You may revise the coding style
always @* begin
    case (state)
        IDLE: begin
            DONE = 0;
            if (START) begin
                state_next = CALC;
                error_next =
                    (A == 0 || B == 0) ? 1'b1 : 0;
            end else begin
                state_next = IDLE;
                error_next = 0;
            end
        end
    endcase
end
```

```
        CALC: begin
            // [lab] finish this block
            //
        end
        FINISH: begin
            // [lab] finish this block
            //         DONE =
            //         error_next =
            //         state_next =
        end
        default: begin
            DONE = 0;
            state_next = IDLE;
            error_next = 0;
        end
    endcase
end
endmodule
```

Lab Template: gcd_t.v (1/2)

 

```
module stimulus;
  parameter cyc = 10;
  parameter delay = 1;

  reg clk, rst_n, start;
  reg [7:0] a, b;
  wire done, error;
  wire [7:0] y;


  GCD gcd01 (
// [lab] complete the port connections
//   .CLK(...)
//   .RST_N(
//   ...
//   ...
  );
```

```
always #(cyc/2) clk = ~clk;

initial begin
  $fsdbDumpfile("gcd.fsdb");
  $fsdbDumpvars;

  $monitor($time, " CLK=%b RST_N=%b
START=%b A=%d B=%d | DONE=%b Y=%d
ERROR=%b",
          clk, rst_n, start, a, b, done, y,
error);
end
```

Lab Template: gcd_t.v (2/2)

 

```
initial begin
    clk = 1;
    rst_n = 1;
    #(cyc);
    #(delay) rst_n = 0;
    #(cyc*4) rst_n = 1;
    #(cyc*2);

    #(cyc) nop;


    #(cyc) load; data_in(8'd21, 8'd6);
    #(cyc) nop;
    @(posedge done);

// [lab] apply more patterns to cover
// different conditions

    #(cyc) nop;
    #(cyc*8);
    $finish;
end
```


```
// take a careful look at
// the usage of task here
task nop;
    begin
        start = 0;
    end
endtask
task load;
    begin
        start = 1;
    end
endtask
task data_in;
    input [7:0] data1, data2;
    begin
        a = data1;
        b = data2;
    end
endtask
endmodule
```

Simulation

 

- Syntax checking
`ncverilog -c gcd.v`
- Verilog simulation
`ncverilog gcd_t.v gcd.v`
- Using Makefile
`make`
`make clean`
`make veryclean`
- Debugging using waveform viewer
`nWave`

Guideline of Design Procedure

 


- Prepare the block diagram and FSM carefully
- Try to symbolize every condition for
 - State transitions
 - Mode selection for datapath
- FSM: the simpler the better
 - One single state can take multiple cycles
 - States can be nested
- Design should be done before Verilog coding
- There is no one BEST style for every design
 - State arrangement
 - Naming convention

Lab Requirement (1/2)



- Part A
 - Complete the Verilog RTL design
 - Simulation using Makefile
 - Try to cover as many input conditions as you can to verify the functionality
 - Explain your selection of test patterns
 - Debugging the timing using waveform viewer nWave
 - [Optional] Is there any room of improvement regarding to the timing?

Lab Requirement (2/2)

 

- Part B
 - Extend your design to support GCD calculation of two 16-bit positive integers
 - The I/O names and widths remain the same
 - A , B , and Y are still 8-bit signals
 - You need two cycles to complete the data transfer
 - E.g., the 1st cycle: $A[15:8]$; the 2nd cycle: $A[7:0]$
 - Now *START* and *DONE* are two-cycle signals
 - Assume they are asserted for two consecutive cycles
 - [Optional] Can you support the control with two separate active cycles?
 - [Optional] Is there any room of improvement regarding to the timing?
- Write a summary report